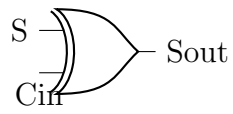


1 Half-adder

For a half adder we get an exclusive OR gate for the sum and an AND gate for the carry.
for a full adder, we get two half adders and an OR gate.

Cout



C

