Lab 10: Three-out-of-Four Detection

Arturo Salinas-Aguayo
CSE 2301: Principles and Practice of Digital Logic Design Dr. Mohammad Khan, Section 003L-1248 Electrical and Computer Engineering Department



Flip Flop Question

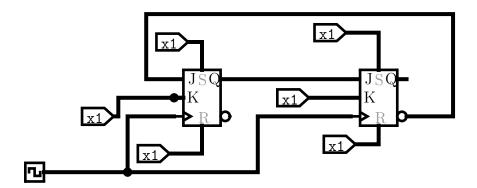


Table 1: Table from Circuit

CURRENT						NEXT	
Q_b	Q_a	J_B	K_B	J_A	K_A	Q_b	Q_a
0	0	0	0	1	1	0	1
0	1	1	0	1	1	1	0
1	0	0	0	0	1	1	0
1	1	1	0	0	1	1	0

Discussion

Practice Questions